



Maritime University of Szczecin
Faculty of Marine Engineering
Department of Physics and Chemistry



Physics Laboratory

Laboratory Manual

Determining the resonance in a series RLC connection

English version written by
dr Agata Kowalska


Szczecin 2018

Equipment:

1. PW-13 generator.
2. MRA-2 resonant circuit.
3. Two multimeters.

Exercise:

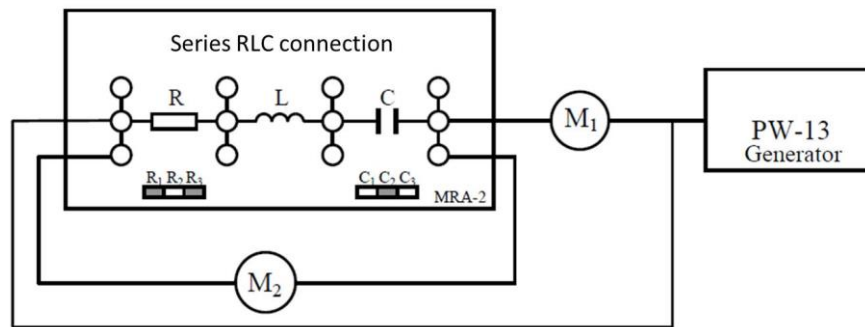1. Check if the circuit is set according to the scheme:



- PW-13 generator: generator multiplier $\cdot 1$, voltage range 10 V,
 - MRA-2 resonant circuit: pushed switches: R_1 and C_2 ,
 - multimeter M_1 : set on the AC – 20 mA range,
 - multimeter M_2 : switch in the “FREQ” position.
2. Turn on the generator and multimeters. Set the frequency of the generator so that the M_2 meter showed $f = 1000$ Hz. Using the “OUTPUT VOLTAGE” potentiometer (it can be found on the generator), set the value of the voltage supplying the resonant circuit on $U = 3$ V (we always read the value of the voltage in the upper right part of the window of the M_2 meter. The same meter indicates the frequency).
 3. Examine the dependence of current I flowing in the R_1LC_2 circuit from the frequency f in the 1000 – 9000 Hz range. During the measurements keep a constant value of the power supply voltage $U = 3.000 \pm 0.010$ V, by adjusting its value with the “OUTPUT VOLTAGE” potentiometer.
 4. On the basement of the obtained results, specify the frequency range in which the resonant frequency occurs. Then, changing the frequency f , determine with an accuracy of 10 Hz its resonance value – at this value current reaches the maximum.
 5. Examine the dependence of current I flowing in the R_1LC_2 circuit from the frequency f in the $(f_r - 1000, f_r + 1000)$ Hz range, every 200 Hz. During the measurements keep a constant value of the power supply voltage $U = 3.000 \pm 0.010$ V, by adjusting its value with the “OUTPUT VOLTAGE” potentiometer.
 6. Repeat steps described in steps 3 – 5 for R_2LC_2 and R_1LC_3 systems.
 7. Set the generator frequency to 1000 Hz.
 8. On one graph draw dependencies $I(f)$ for all examined RLC systems. Draw the trend lines in the charts to form resonance curves.
 9. From the obtained graphs, read the current I_r in resonance and frequencies f_1, f_2 and f_r . calculate the angular frequencies:

