



**Maritime University of Szczecin**  
**Faculty of Marine Engineering**  
**Department of Physics and Chemistry**



**Physics Laboratory**

**Laboratory Manual**

**Verification of Ohm's law for DC (direct current) circuits**

English version written by  
dr Agata Kowalska


Szczecin 2018

**Equipment:**

1. DC power supply.
2. Multimeter.
3. Two resistors.

**Exercise:**

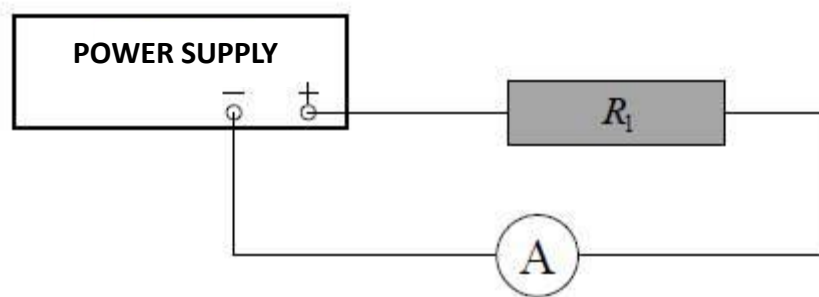1. Set the CURRENT knob on the power supply to the rightmost position and FINE and VOLTAGE to the most left position.
2. Set multimeter to 200 mA DC range.
3. Connect the circuit according to the diagram:



4. Turn on the power supply.
5. Adjusting the position of fine and voltage knobs set the supply voltage from  $U_{MIN} = 1 \text{ V}$  to  $U_{MAX} = 10 \text{ V}$  increasing by 1V. Record the voltage values displayed on the power supply and current values indicated by the ammeter.
6. Set the voltage  $U = 0 \text{ V}$ . Turn off the power supply and the multimeter.
7. Repeat steps 2 – 6 using:
  - a. resistor  $R_2$ ,
  - b. resistors  $R_1$  and  $R_2$  connected in series,
  - c. resistors  $R_1$  and  $R_2$  connected in parallel, instead of resistor  $R_1$ .
8. In one graph present the dependence of  $I$  on  $U$  for all examined systems.
9. Applying the linear regression method:

$$I = \frac{1}{R} \cdot U$$

$$y = a \cdot x + b$$

find the resistance of individual resistors  $R_1$  and  $R_2$  as well as the resistance of resistors connected in series  $R_S$  and connected in parallel  $R_R$ .

10. Using formulas:

$$R'_S = R_1 + R_2,$$

$$R'_R = \frac{R_1 R_2}{R_1 + R_2}$$

calculate the resistance of series and parallel connections. Compare resistance values  $R'_S$  and  $R'_R$  with values  $R_S$  and  $R_R$  obtained previously. Write down the conclusions.

**Measuring table:**

$R_1$		$R_2$		$R_1$ and $R_2$ connected in series		$R_1$ and $R_2$ connected in parallel	
$U$ [V]	$I$ [mA]	$U$ [V]	$I$ [mA]	$U$ [V]	$I$ [mA]	$U$ [V]	$I$ [mA]

$R_1 = \dots\dots\dots \Omega$

$R_2 = \dots\dots\dots \Omega$

$R_S = \dots\dots\dots \Omega$

$R_R = \dots\dots\dots \Omega$

$R'_S = \dots\dots\dots \Omega$

$R'_R = \dots\dots\dots \Omega$